



Computer Organization (1) - Spring Semester - 2021/2022

Home > My courses > Computer Organization (1) - Spring - 2021/2022 > General > Computer Organization (1) - Quiz(2)

Question 1

Not yet answered
Marked out of 1.00
Flag question

How many types of sequential circuits are?

Select one:

- ☐ a. 4
- ☒ b. 2
- ☐ c. 3
- ☐ d. 5

Question 2

Not yet answered
Marked out of 1.00
Flag question

The no. of directed arcs emanating from any state in a state diagram is

Select one:

- ☐ a. $2n$, where n is no. of inputs
- ☒ b. Independent of no. of inputs
- ☐ c. An arbitrary number
- ☐ d. $2n$, where n is n. of flipflops

Question 3

Not yet answered
Marked out of 1.00
Flag question

The truth table for an S-R flip-flop has how many VALID entries?

Select one:

- ☐ a. 2
- ☐ b. 4
- ☒ c. 3
- ☐ d. 1

Question 4

Not yet answered
Marked out of 1.00
Flag question

When is a flip-flop said to be transparent?

Select one:

- ☐ a. when you can see through the IC packaging
- ☐ b. when the Q output is opposite the input
- ☒ c. when the Q output follows the input

Quiz navigation

1	2	3	4
5	6	7	8
9	10		

[Finish attempt ...](#)

Time left **0:06:40**

Question 5

Not yet answered

Marked out of 1.00

Flag question

D flip flop is said transparent when

Select one:

- ☐ a. output is low
- ☐ b. output follows clock
- ☒ c. output follows input
- ☐ d. output is high

Question 6

Not yet answered

Marked out of 1.00

Flag question

The term synchronous refers to events that do not occur at the same time.

Select one:

- ☐ True
- ☒ False

Question 7

Not yet answered

Marked out of 1.00

Flag question

Assume a J-K flip-flop has 1s on the J and K inputs. The next clock pulse will cause the output to _____.

Select one:

- ☐ a. latch
- ☐ b. set
- ☐ c. reset
- ☒ d. toggle

Question 8

Not yet answered

Marked out of 1.00

Flag question

In state diagram, what does an arrow between the circles indicate?

Select one:

- ☒ a. Next state
- ☐ b. State transition
- ☐ c. Present state
- ☐ d. Don't care condition

Question 9

Not yet answered

Marked out of 1.00

Flag question

A gated S-R flip-flop goes into the SET condition when S is HIGH, R is LOW, and EN is HIGH.

Select one:

- ☒ True
- ☐ False

Question 10

Not yet answered

Marked out of 1.00

A decoder converts n inputs to _____ outputs

Select one:

1.00

Flag
question

Select one:

- ☐ a. n^2
- ☒ b. 2^n
- ☐ c. n^n
- ☐ d. n

Finish attempt ...

Learn Any Time, Any Where
Hotline: 16541

