

# Electronics Section 06

Faculty of Information Technology Egyptian  
E-Learning University

Beni Suef Center & Assiut Center Fall 2021

**By Aya Gamal & Ahmed Abdel-Rahim**

# Capacitors

A **capacitor** consists of two conducting plates separated by an insulator (or dielectric).


**Capacitance** is the ratio of the charge on one plate of a capacitor to the voltage difference between the two plates, measured in farads (F).

$$q = Cv$$

## Calculation of capacitance


### Isolated charged sphere

### Parallel Plates

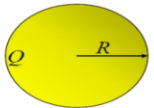

$$C_0 = \frac{R}{k_e} = 4\pi\epsilon_0 R$$

$$k_e = \frac{1}{4\pi\epsilon_0}$$

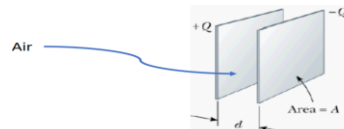

$$C_0 = \frac{\epsilon_0 A}{d}$$

$$\epsilon_0 = 8.854187817 \times 10^{-12} \text{ F/m}$$

## Capacitors with any dielectric

$$C = kC_0$$


K is a dimensionless factor, called the **dielectric constant** where  $C_0$  is the capacitance in the absence of the dielectric

A capacitor is an open circuit to dc.


The voltage on a capacitor cannot change abruptly.

The **equivalent capacitance** of  $N$  parallel-connected capacitors is the sum of the individual capacitances.


$$i = C \frac{dv}{dt}$$

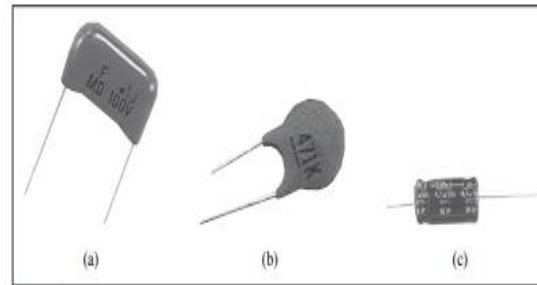


**Figure**  
Fixed capacitors: (a) polyester capacitor, (b) ceramic capacitor, (c) electrolytic capacitor.  
Courtesy of Tech America.

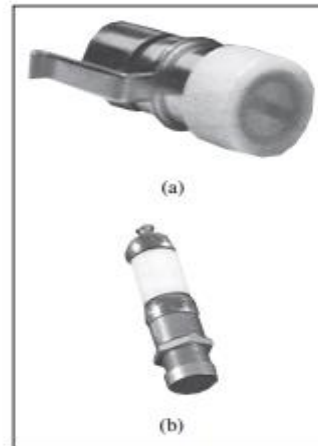


**Figure**  
Variable capacitors: (a) trimmer capacitor, (b) filmtrim capacitor.  
Courtesy of Johanson.

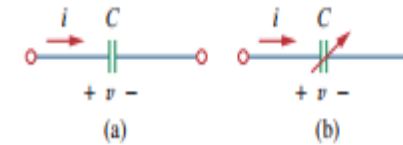


**Figure**  
Circuit symbols for capacitors: (a) fixed capacitor, (b) variable capacitor.

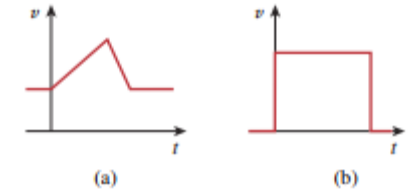

**Figure**  
Voltage across a capacitor: (a) allowed, (b) not allowable; an abrupt change is not possible.

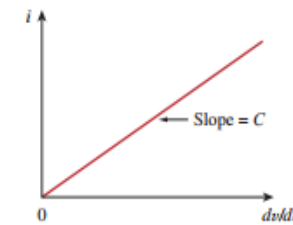

**Figure**  
Current-voltage relationship of a capacitor.

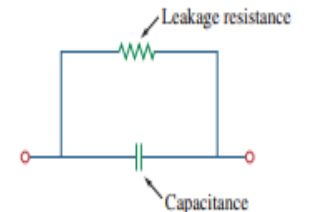

**Figure**  
Circuit model of a nonideal capacitor.

The **equivalent capacitance** of series-connected capacitors is the reciprocal of the sum of the reciprocals of the individual capacitances.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

## Energy stored in charged capacitor


$$U_E = \frac{Q^2}{2C} = \frac{1}{2} Q \Delta V = \frac{1}{2} C (\Delta V)^2$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

# Inductors

An **inductor** consists of a coil of conducting wire.

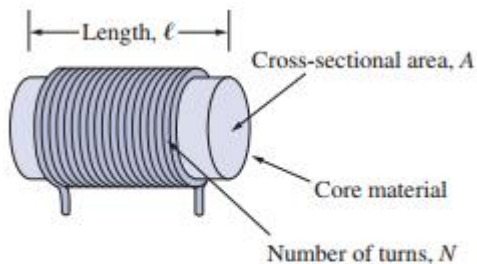

**Figure 6.21**  
Typical form of an inductor.

$$L = \frac{N^2 \mu A}{\ell} \quad \mu = \mu_r \mu_0$$

$L$  = Inductance of coil in Henrys

$N$  = Number of turns in wire coil (straight wire = 1)

$\mu$  = Permeability of core material (absolute, not relative)

$\mu_r$  = Relative permeability, dimensionless ( $\mu_0 = 1$  for air)

$\mu_0 = 1.26 \times 10^{-6}$  T-m/A permeability of free space

$A$  = Area of coil in square meters =  $\pi r^2$

$\ell$  = Average length of coil in meters

An inductor acts like a short circuit to dc.

The current through an inductor cannot change instantaneously.


$$L = \frac{\Phi}{i} = \frac{vt}{i}$$

$$v = L \frac{di}{dt}$$

$$w = \frac{1}{2} Li^2$$


The **equivalent inductance** of parallel inductors is the reciprocal of the sum of the reciprocals of the individual inductances.

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots + \frac{1}{L_N}$$

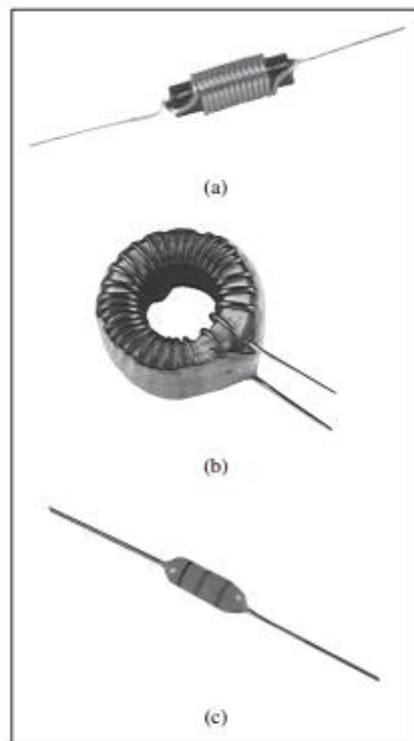


**Figure**  
Various types of inductors: (a) solenoidal wound inductor, (b) toroidal inductor, (c) chip inductor.  
Courtesy of Tech America.


**Inductance** is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in henrys (H).

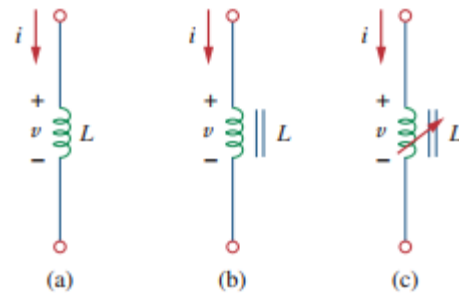

**Figure**  
Circuit symbols for inductors: (a) air-core, (b) iron-core, (c) variable iron-core.

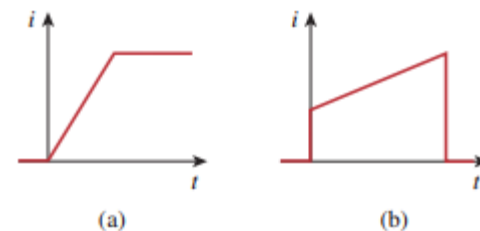


**Figure**  
Current through an inductor: (a) allowed, (b) not allowable; an abrupt change is not possible.

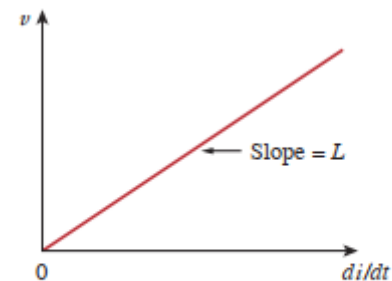

**Figure**  
Voltage-current relationship of an inductor.

Since an inductor is often made of a highly conducting wire, it has a very small resistance.

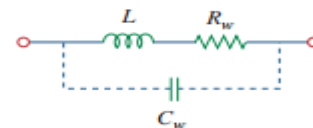

**Figure**  
Circuit model for a practical inductor.

The **equivalent inductance** of series-connected inductors is the sum of the individual inductances.

$$L_{eq} = L_1 + L_2 + L_3 + \cdots + L_N$$


**Q1.** If the voltage across a 7.5-F capacitor is  $2t e^{-3t}$  V, find the current and the power.

### Solution

$$i = C \frac{dv}{dt} = 7.5(2e^{-3t} - 6te^{-3t}) = 15(1 - 3t)e^{-3t} \text{ A}$$

$$p = vi = 15(1-3t)e^{-3t} \cdot 2t e^{-3t} = 30t(1 - 3t)e^{-6t} \text{ W}.$$

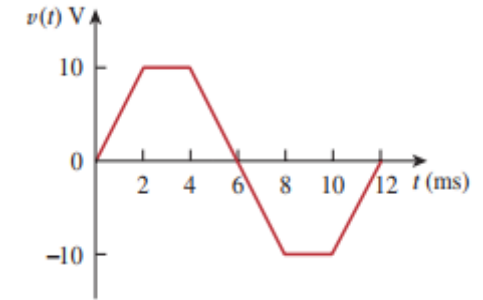**Q2.** The voltage waveform in the Figure is applied across a **55-μF** capacitor. Draw the current waveform through it.



## Solution


$$i = C \frac{dv}{dt} = 55 \times 10^{-6} \text{ times the slope of the waveform.}$$

For example, for  $0 < t < 2$ ,


$$\frac{dv}{dt} = \frac{10}{2 \times 10^{-3}}$$

$$i = C \frac{dv}{dt} = (55 \times 10^{-6}) \frac{10}{2 \times 10^{-3}} = 275 \text{ mA}$$

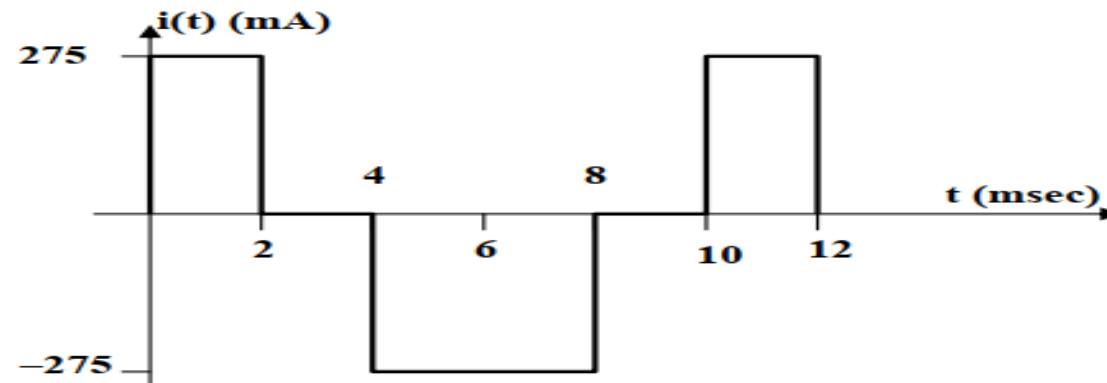Thus the current  $i(t)$  is sketched below.




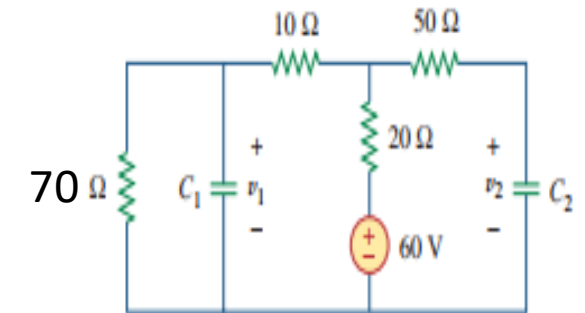**Q3.** Find the voltage across the capacitors in the circuit of the Figure under dc conditions.


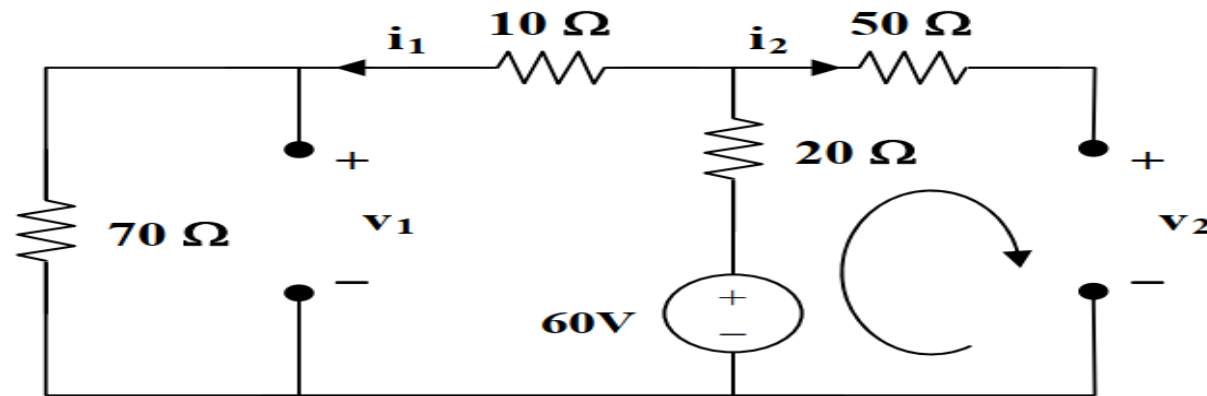
### Solution

Under dc conditions, the circuit becomes that shown below:




$$i_2 = 0, i_1 = 60/(70+10+20) = 0.6 \text{ A}$$

$$v_1 = 70i_1 = 42 \text{ V}, v_2 = 60 - 20i_1 = 48 \text{ V}$$


$$\text{Thus, } v_1 = 42 \text{ V}, v_2 = 48 \text{ V.}$$

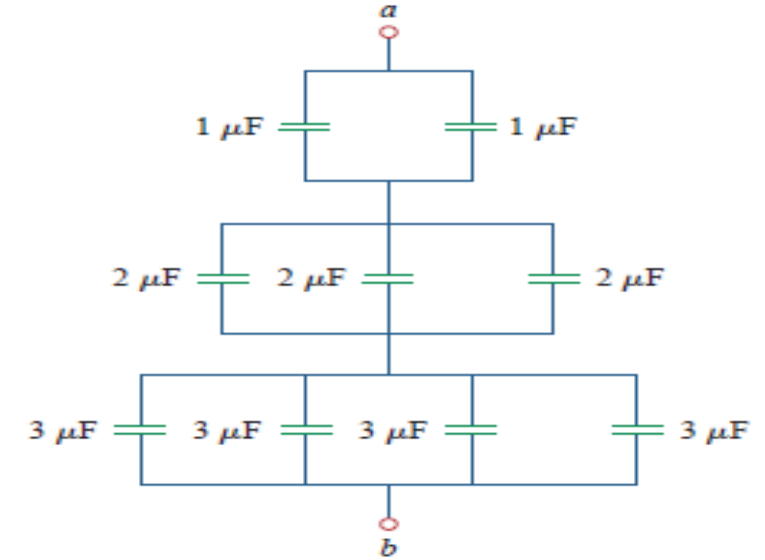**Q4.** Find the equivalent capacitance at terminals a-b of the circuit in the figure.



## Solution

Consider the circuit shown below.

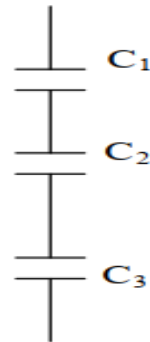

$$C_1 = 1 + 1 = 2 \mu F$$


$$C_2 = 2 + 2 + 2 = 6 \mu F$$

$$C_3 = 4 \times 3 = 12 \mu F$$

$$1/C_{eq} = (1/C_1) + (1/C_2) + (1/C_3) = 0.5 + 0.16667 + 0.08333 = 0.75 \times 10^{-6}$$

$$C_{eq} = \mathbf{1.3333 \mu F.}$$

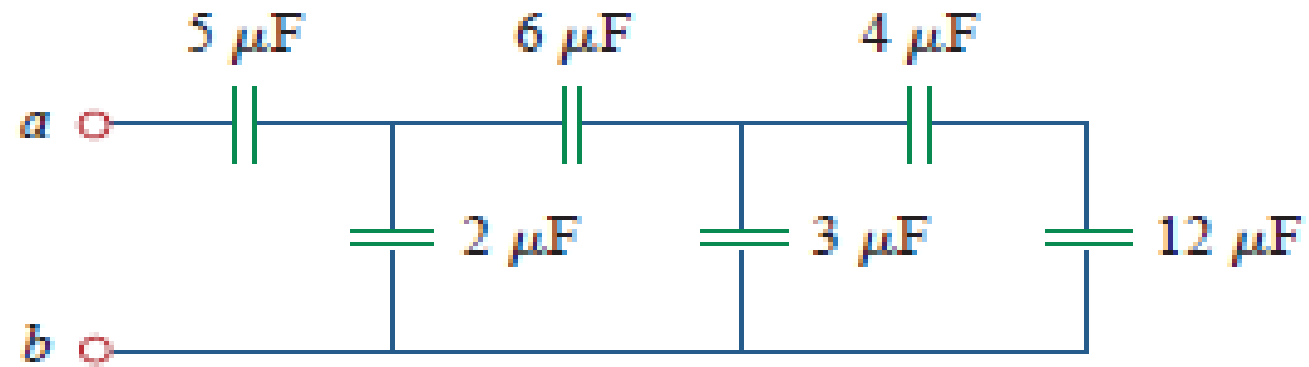**Q5.** Determine the equivalent capacitance at terminals a – b of the circuit in the Figure.



**Solution**

$4\ \mu\text{F}$  in series with  $12\ \mu\text{F} = (4 \times 12) / 16 = 3\ \mu\text{F}$

$3\ \mu\text{F}$  in parallel with  $3\ \mu\text{F} = 6\ \mu\text{F}$

$6\ \mu\text{F}$  in series with  $6\ \mu\text{F} = 3\ \mu\text{F}$

$3\ \mu\text{F}$  in parallel with  $2\ \mu\text{F} = 5\ \mu\text{F}$

$5\ \mu\text{F}$  in series with  $5\ \mu\text{F} = 2.5\ \mu\text{F}$

Hence  $C_{\text{eq}} = 2.5\ \mu\text{F}$



**Q6.** The current through a 10-mH inductor is  $10 e^{-t/2}$  A. Find the voltage and the power at  $t = 3$  s

**Solution**

$$i = 10e^{-t/2}$$


$$\begin{aligned} v &= L \frac{di}{dt} = 10 \times 10^{-3} (10) \left( \frac{1}{2} \right) e^{-t/2} \\ &= -50e^{-t/2} \text{ mV} \end{aligned}$$

$$v(3) = -50e^{-3/2} \text{ mV} = \mathbf{-11.157 \text{ mV}}$$

$$p = vi = -500e^{-t} \text{ mW}$$


$$p(3) = -500e^{-3} \text{ mW} = \mathbf{-24.89 \text{ mW}}.$$

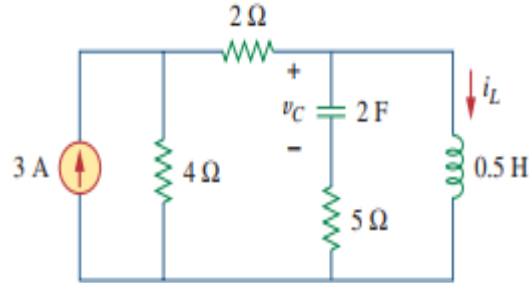**Q7.** Find  $v_C$ ,  $I_L$  and the energy stored in the capacitor and inductor in the circuit of the Figure under dc conditions.


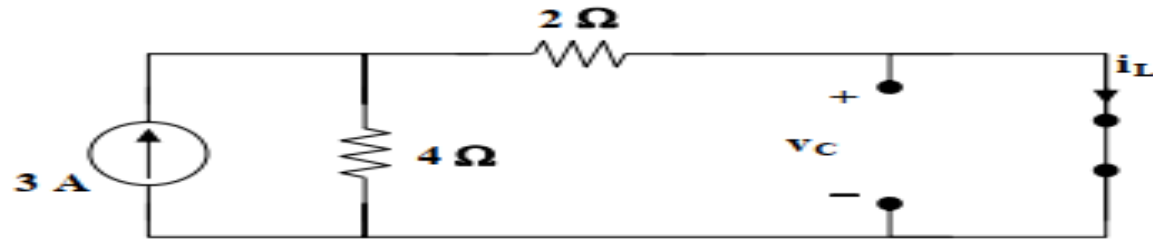
### Solution

Under dc conditions, the circuit is as shown below:




By current division,

$$i_L = \frac{4}{4+2}(3) = 2\text{A}, \quad v_C = 0\text{V}$$

$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} \left( \frac{1}{2} \right) (2)^2 = 1\text{J}$$


$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} (2)(0) = 0\text{J}$$

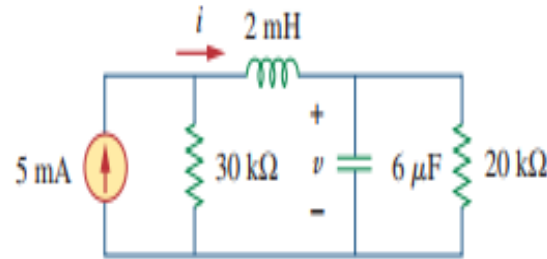**Q8.** Under steady-state dc conditions, find  $i$  and  $v$  in the circuit in Figure.


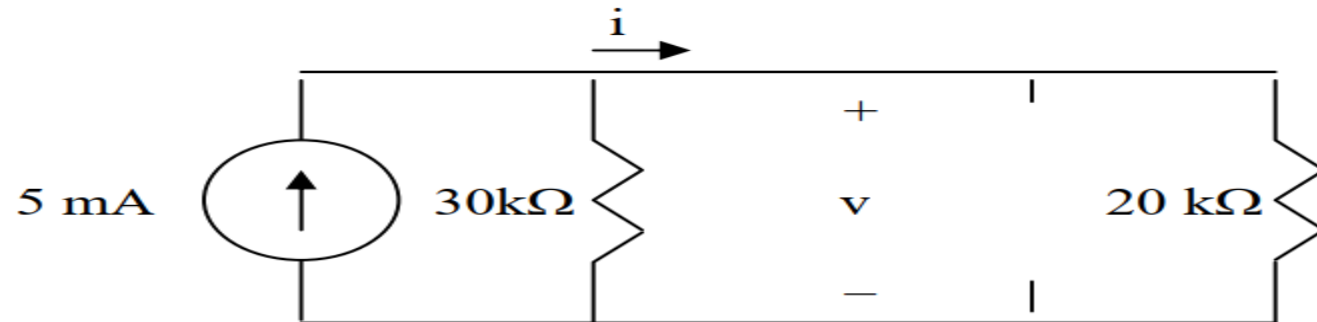
### Solution

Under steady-state, the inductor acts like a short-circuit, while the capacitor acts like an open circuit as shown below.




Using current division,

$$i = (30\text{k}/(30\text{k}+20\text{k}))(5\text{mA}) = \mathbf{3 \text{ mA}}$$

$$v = 20\text{k}i = \mathbf{60 \text{ V}}$$

**Q9.** An energy-storage network consists of series- connected 16-mH and 14mH inductors; in parallel with series-connected 24-mH and 36-mH inductors. Calculate the equivalent inductance.

**Solution**

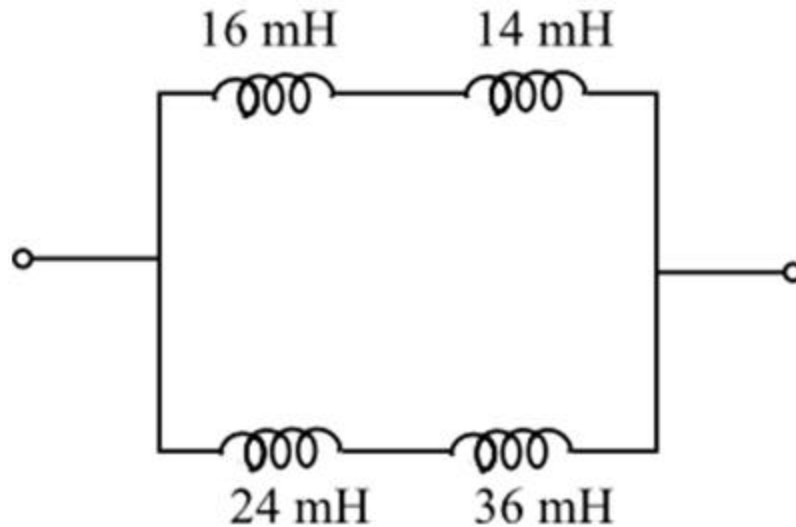


16mH in series with 14 mH =  $16+14=30$  mH

24 mH in series with 36 mH =  $24+36=60$  mH

30mH in parallel with 60 mH =  $30 \times 60 / 90 = \mathbf{20 \text{ mH}}$

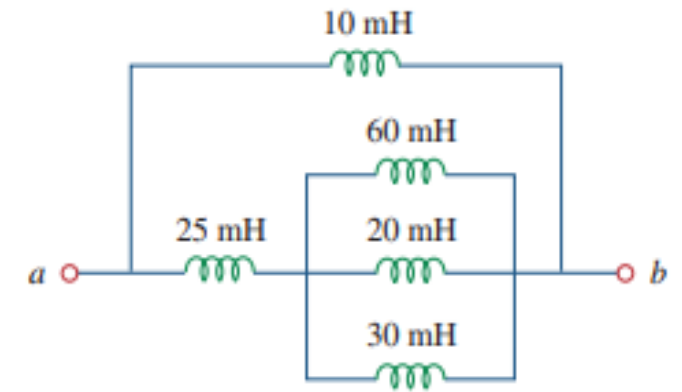**Q10.** Determine  $L_{eq}$  *equivalent* at terminals a-b of the circuit in the figure.



**Solution**

$$\frac{1}{L} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10}$$

$$L = 10 \text{ mH}$$

$$L_{eq} = 10 \parallel (25 + 10) = \frac{10 \times 35}{45}$$

$$= 7.778 \text{ mH}$$

## MCQ

1) By what factor is the capacitance of a metal sphere multiplied if its volume is tripled?

- (a) 3
- (b)  $3^{1/3}$
- (c) 1
- (d)  $3^{-\frac{1}{3}}$
- (e)  $\frac{1}{3}$

**Answer: B**