

Section (9)

Physics II

“Resistances and their connections”

- In Ohm's Law, the current is directly proportional to the voltage and the proportionality constant is called "Resistance"

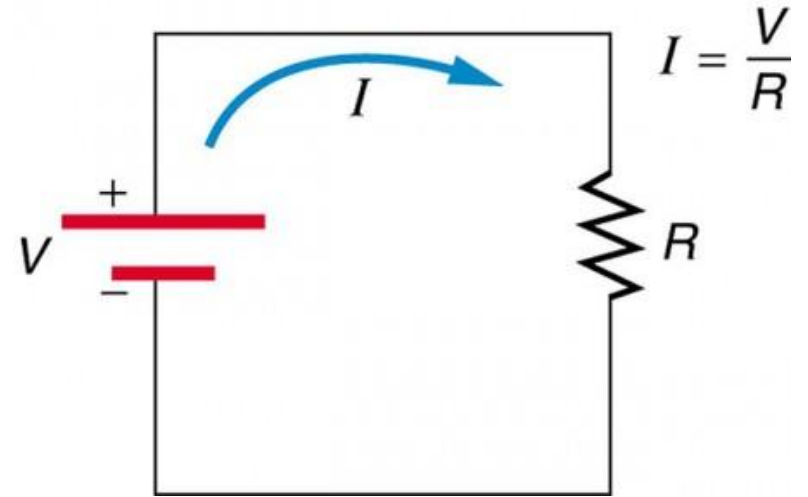
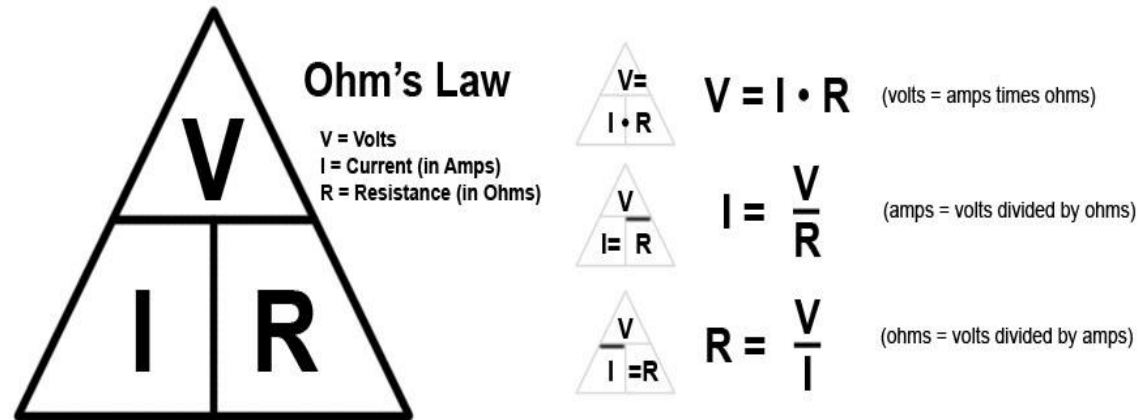



Fig (1)

Example 1 :

What is the resistance of an automobile headlight through which 2.50 A flows when 12.0 V is applied to it?

(Solution)
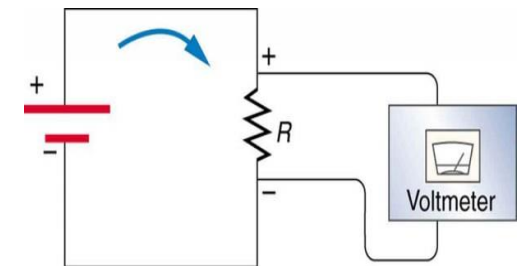
$$R = \frac{V}{I} = \frac{12.0 (V)}{2.50 (A)} = 4.80 \Omega$$



But when it comes to more than a single resistance, our calculations will be a bit different and will depend on the type of the connections between the resistances such as:

Series connection


Parallel connection

1- Series connection of resistors:

Current: $I_{Total} = I_{R_1} = I_{R_2} = \dots$

Equivalent resistance $R_{total} = R_1 + R_2 + R_3 + \dots + R_n$ etc.

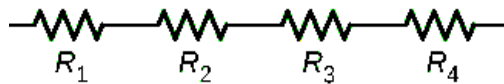Voltage: $V_{Total} = V_{R_1} + V_{R_2} + V_{R_3} + \dots + V_N$



(a) Resistors connected in series


Fig(2)

2- Parallel connection of resistors:

Current: $I_{Total} = I_1 + I_2 + I_3 + \dots + I_n$

Equivalent resistance: $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$ etc

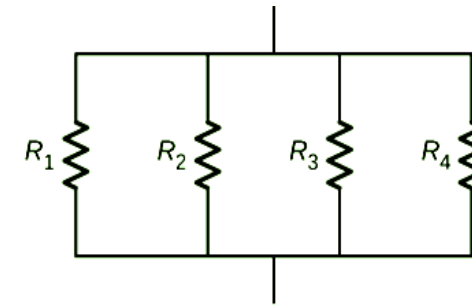Voltage: $V_{Total} = V_{R_1} = V_{R_2} = V_{R_3} = V_{R_n}$



(b) Resistors connected in parallel

Fig(3)

➡ For the case of two resistances in parallel connection

$$R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$

Example2:

Using Ohms Law, calculate the equivalent series resistance, the series current, voltage drop and power for each resistor in the following resistors in series circuit.

(Solution)

$$R_{eq} = R_1 + R_2 + R_3 \quad R_{eq} = 10 + 20 + 30 = 60\Omega$$


$$I = I_{R_1} = I_{R_2} = I_{R_3} = \frac{V_{total}}{R_{eq}} \quad I (A) = \frac{12 (V)}{60 (\Omega)} = 200 \text{ mA} = 0.2 \text{ A}$$

$$V_1 = R_1 I = 10 \times 0.2 = 2 \text{ V} , V_2 = R_2 I = 20 \times 0.2 = 4 \text{ V} , V_3 = R_3 I = 30 \times 0.2 = 6 \text{ V}$$

$$V_{total} = V_1 + V_2 + V_3 = 2 + 4 + 6 = 12 \text{ V}$$

$$P_1 = V_1 I = 2 \times 0.2 = 0.4 \text{ W} , P_2 = V_2 I = 4 \times 0.2 = 0.8 \text{ W} , P_3 = V_3 I = 6 \times 0.2 = 1.2 \text{ W}$$

$$P_{total} = P_1 + P_2 + P_3 = 0.4 + 0.8 + 1.2 = 2.4 \text{ W}$$

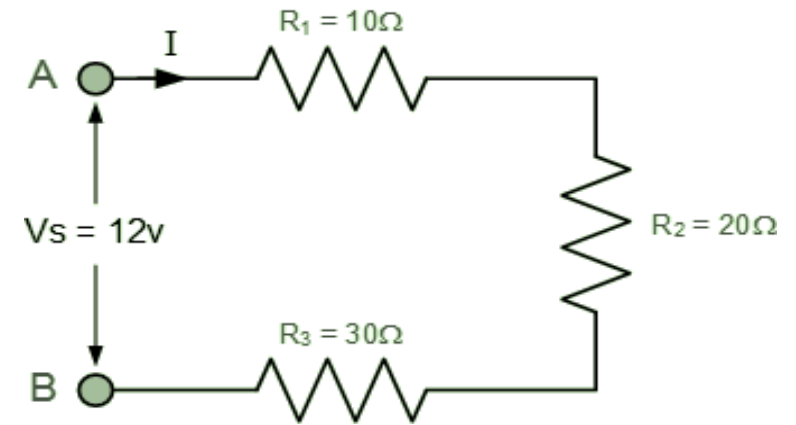

Example 3:

Consider the following circuit which has only two resistors in a parallel combination, knowing that $R_1 = 22\text{ k}\Omega$, and $R_2 = 47\text{ k}\Omega$, Calculate the total or the equivalent resistance of the following circuit.

Solution


Using our formula above for two resistors connected together in parallel we can calculate the total circuit resistance, R_T as:

$$R_T = \frac{22\text{k}\Omega \times 47\text{k}\Omega}{22\text{k}\Omega + 47\text{k}\Omega} = 14,985\Omega \text{ or } 15\text{k}\Omega$$

Another solution:

$$\frac{1}{R_T} = \frac{1}{R_a} + \frac{1}{R_b} = \frac{1}{22\text{k}\Omega} + \frac{1}{47\text{k}\Omega}$$

then $R_T = 15\text{k}\Omega$

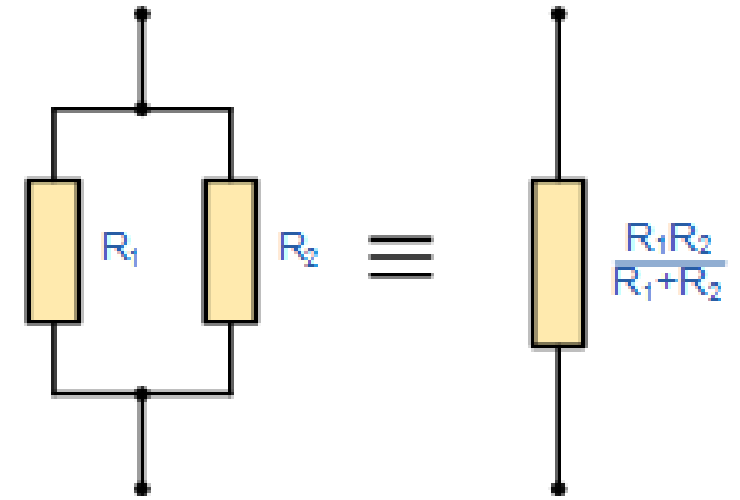

Example 4:

in the following circuit calculate the total current (I_T) taken from the 12v supply.


Solution

$$R_2 + R_3 = 8\Omega + 4\Omega = 12\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_A} + \frac{1}{R_4} = \frac{1}{12} + \frac{1}{12} = 0.1667\Omega^{-1}$$

$$R_{eq} = \frac{1}{0.1667} = 6\Omega$$
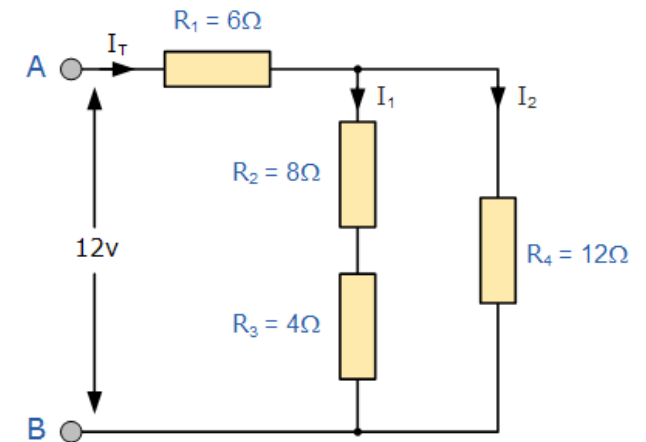
$$R_{(ab)} = R_{eq} + R_1 = 6\Omega + 6\Omega = 12\Omega$$



$$\text{Circuit Current (I)} = \frac{V}{R} = \frac{12}{12} = 1 \text{ Ampere}$$

$$V_{R_1} = I \times R_1 = 1 \times 6 = 6 \text{ V}$$


$$V_{R_a} = I \times R_4 = (12 - V_{R_1}) = 12 - 6 = 6 \text{ V}$$

$$I_1 = 6 \text{ V} \div R_A = 6 \div 12 = 0.5 \text{ A or } 500 \text{ mA}$$

$$I_2 = 6 \text{ V} \div R_4 = 6 \div 12 = 0.5 \text{ A or } 500 \text{ mA}$$

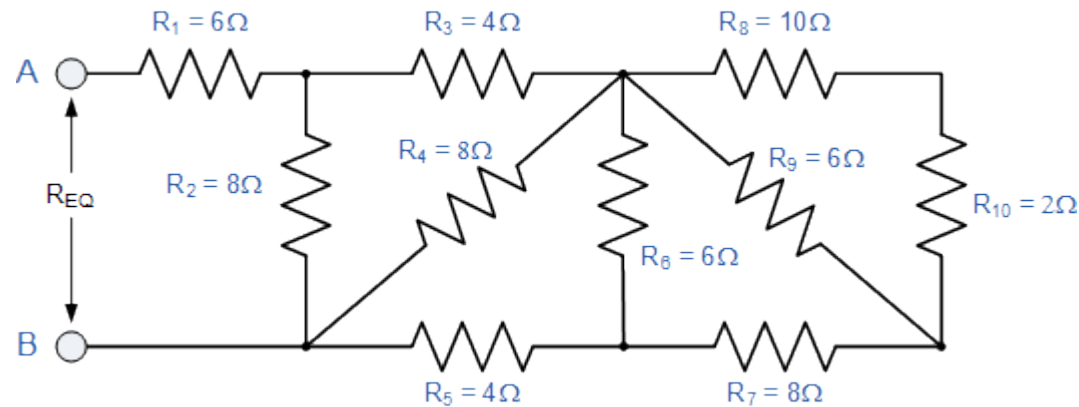
Example 5:

Find the equivalent resistance, R_{EQ} for the following resistor combination circuit.




Solution

1)

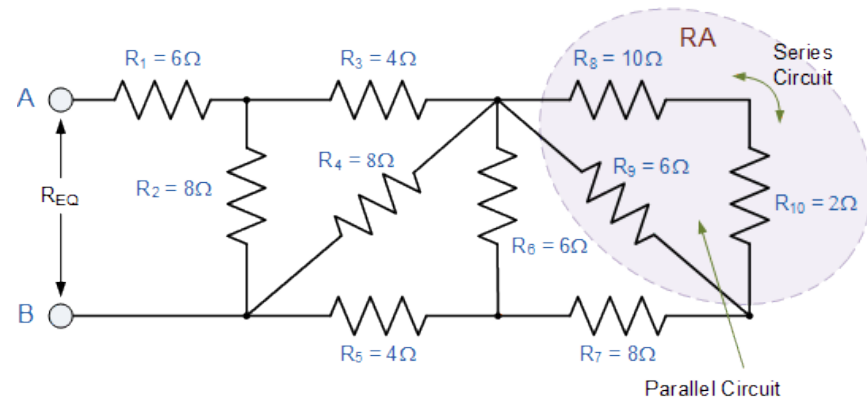


$$R_A = \frac{R_9 \times (R_8 + R_{10})}{R_9 + R_8 + R_{10}} = \frac{6 \times (10 + 2)}{6 + 10 + 2} = 4\Omega$$

3)

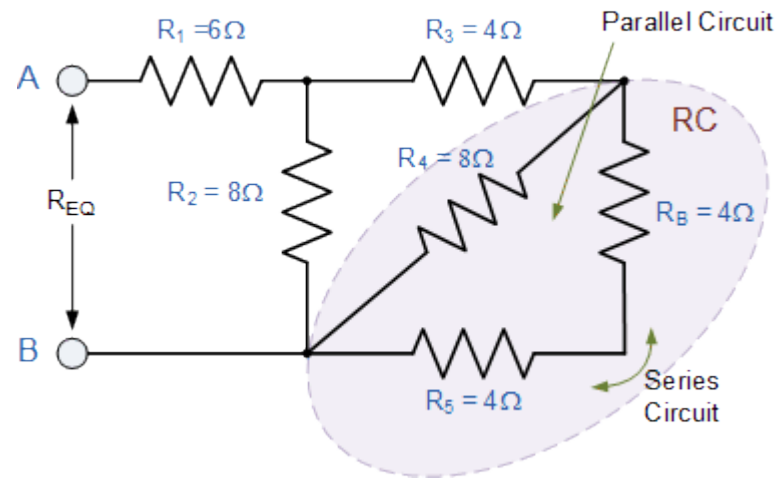


$$R_C = \frac{R_4 \times (R_B + R_5)}{R_4 + R_B + R_5} = \frac{8 \times (4 + 4)}{8 + 4 + 4} = 4\Omega$$

2)

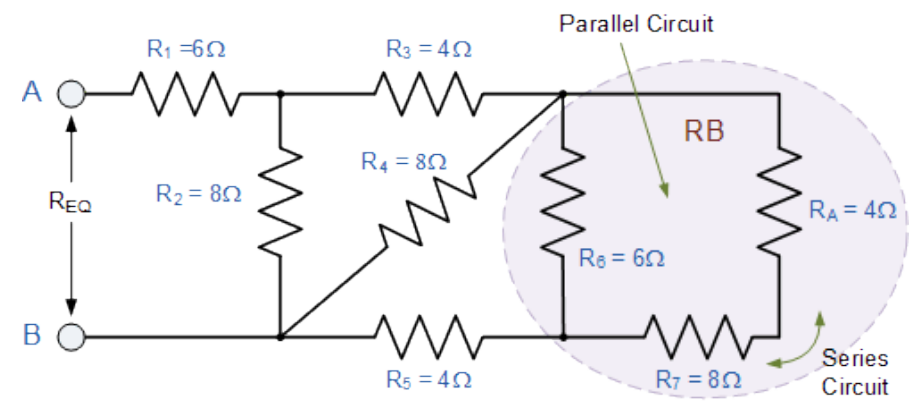


$$R_B = \frac{R_6 \times (R_A + R_7)}{R_6 + R_A + R_7} = \frac{6 \times (4 + 8)}{6 + 4 + 8} = 4\Omega$$

4)

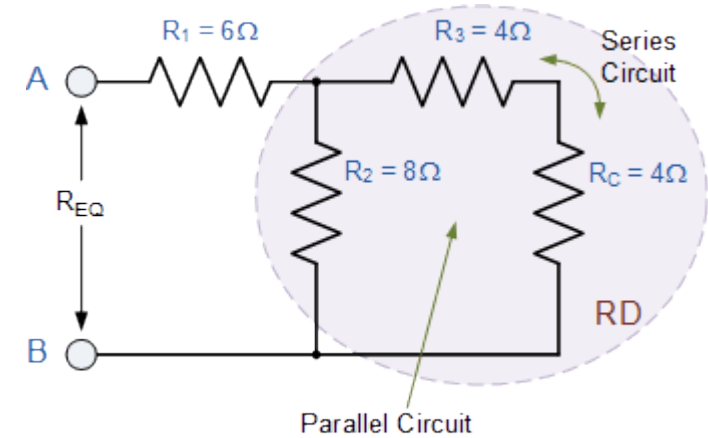

$$R_D = \frac{R_2 \times (R_C + R_3)}{R_2 + R_C + R_3} = \frac{8 \times (4 + 4)}{8 + 4 + 4} = 4\Omega$$


5)

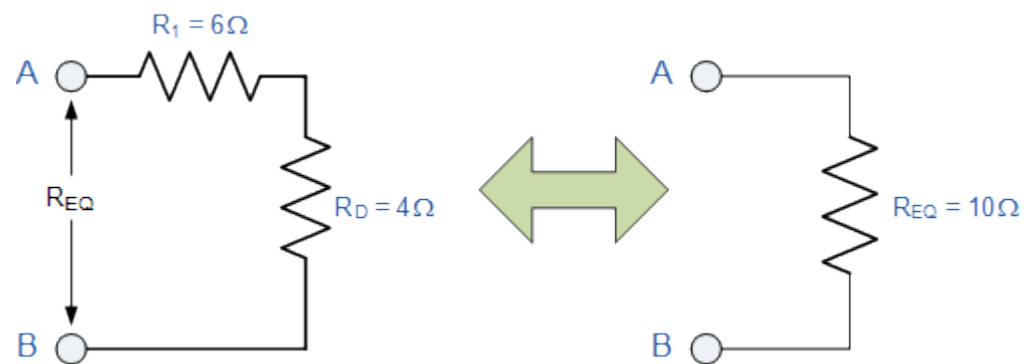

Kirchhoffs Circuit Law

1st KVL

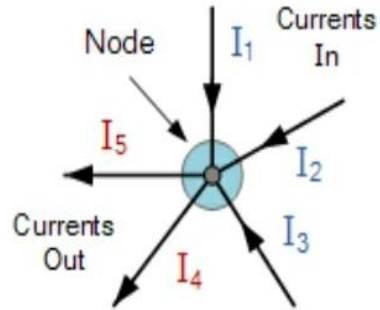
Currents Entering the Node
Equals
Currents Leaving the Node



$$I_1 + I_2 + I_3 + (-I_4 + -I_5) = 0$$

2nd KVL

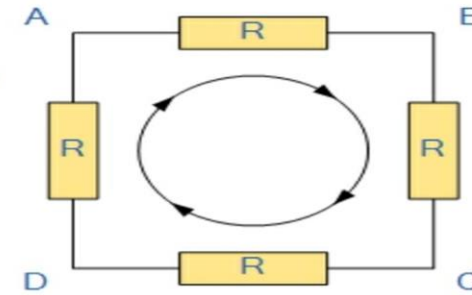
The sum of all the Voltage
Drops around the loop
is equal to Zero



$$V_{AB} + V_{BC} + V_{CD} + V_{DA} = 0$$

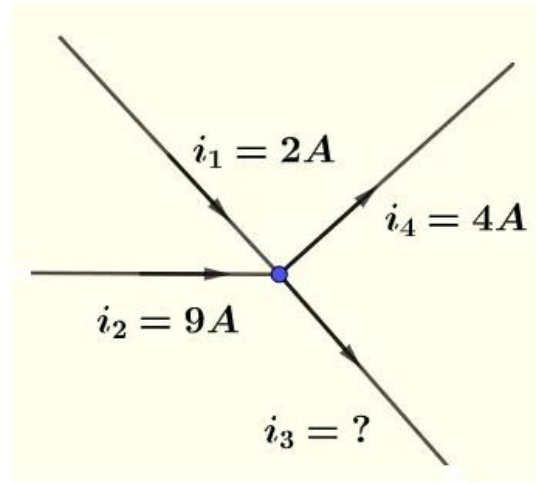Example6:

Find current i_3 at the node shown below.



Solution

Currents i_1 and i_2 are flowing into the node and currents i_3 and i_4 are flowing out of the node. Apply Kirchhoff's law of current at the given node.

$$i_1 + i_2 = i_3 + i_4$$


Substitute the known quantities

$$2 + 9 = i_3 + 4$$

Solve for i_3

$$i_3 = 7A$$

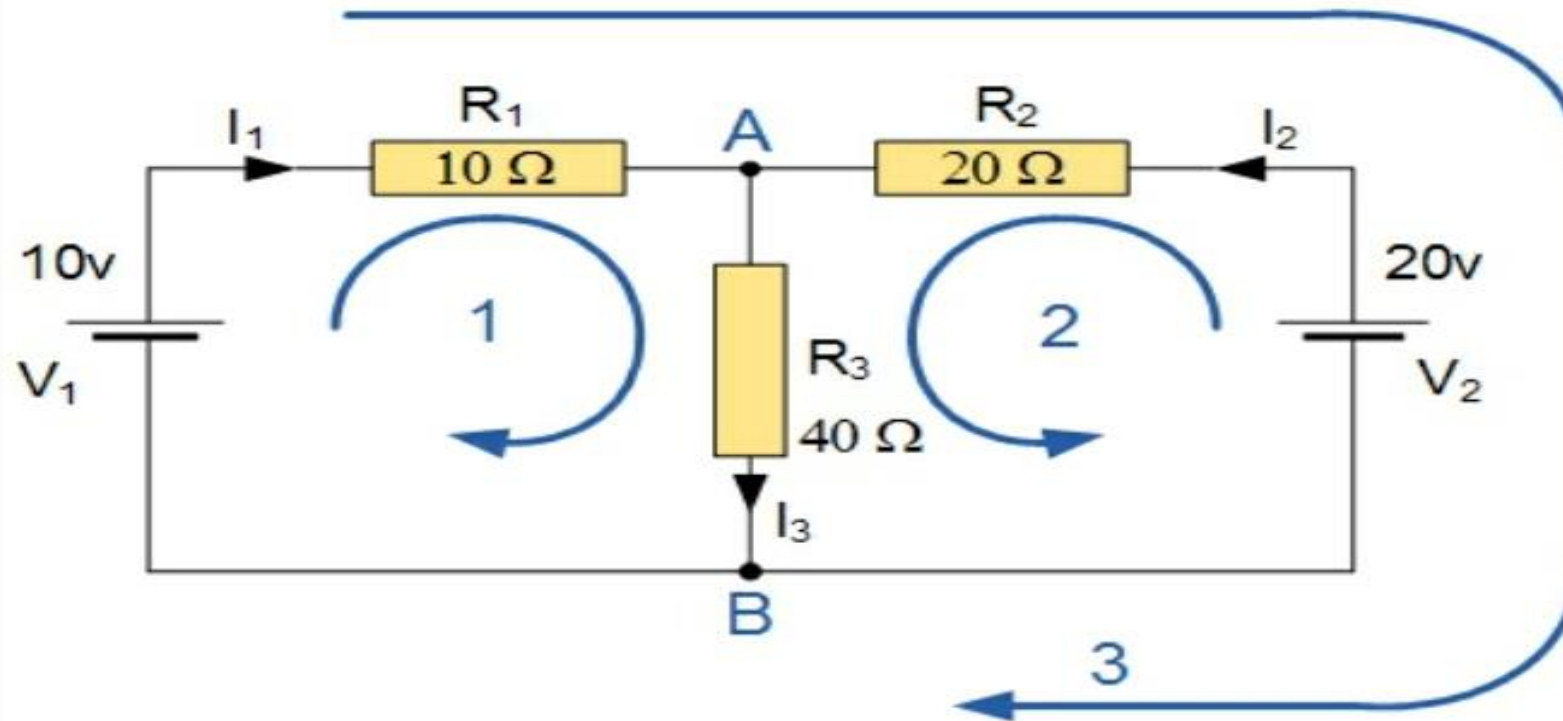Example 7: Determine the voltage across the resistance R_3 and the currents across the following circuit.



Solution

The circuit has 3 branches, 2 nodes (A and B) and 2 independent loops.

Using **Kirchhoffs Current Law, KCL** the equations are given as:

$$\text{At node A: } I_1 + I_2 = I_3$$

$$\text{At node B: } I_3 = I_1 + I_2$$

Using **Kirchhoffs Voltage Law, KVL** the equations are given as:

Loop 1 is given

$$\text{as: } 10 = R_1 I_1 + R_3 I_3 = 10I_1 + 40I_3$$

Loop 2 is given

$$\text{as: } 20 = R_2 I_2 + R_3 I_3 = 20I_2 + 40I_3$$

$$\text{Loop 3 is given as: } 10 - 20 = 10I_1 - 20I_2$$

As I_3 is the sum of $I_1 + I_2$ we can rewrite the equations as;

Eq. No

$$1: 10 = 10I_1 + 40(I_1 + I_2) = 50I_1 + 40I_2$$

Eq. No

$$2: 20 = 20I_2 + 40(I_1 + I_2) = 40I_1 + 60I_2$$

We now have two “**Simultaneous Equations**” that can be reduced to give us the values of I_1 and I_2

Substitution of I_1 in terms of I_2 gives us the value of I_1 as -0.143 Amps

Substitution of I_2 in terms of I_1 gives us the value of I_2 as +0.429 Amps

$$\text{As: } I_3 = I_1 + I_2$$

The current flowing in resistor R_3 is given

$$\text{as: } -0.143 + 0.429 = 0.286 \text{ Amps}$$

and the voltage across the resistor R_3 is given

$$\text{as: } 0.286 \times 40 = 11.44 \text{ volts}$$

The negative sign for I_1 means that the direction of current flow initially chosen was wrong, but never the less still valid. In fact, the 20v battery is charging the 10v battery.

MCQ:

1)What is the maximum power can be generated from an 18-V emf using any combination of a 6.0Ω resistor and a 9.0Ω resistor?

- a)54W
- b)71W
- c)90W
- d)80W

2)Consider a circuit with two unequal resistances in parallel, then...


- a) large current flows in large resistor
- b) current is same in both
- c) potential difference across each is same
- d) smaller resistance has smaller conductance

3)Correct form of ohm's law

- a) $I = VR$
- b) $V \propto I$
- c) $V = IR$
- d) $V = \frac{I}{R}$

4) Find R in the following circuit

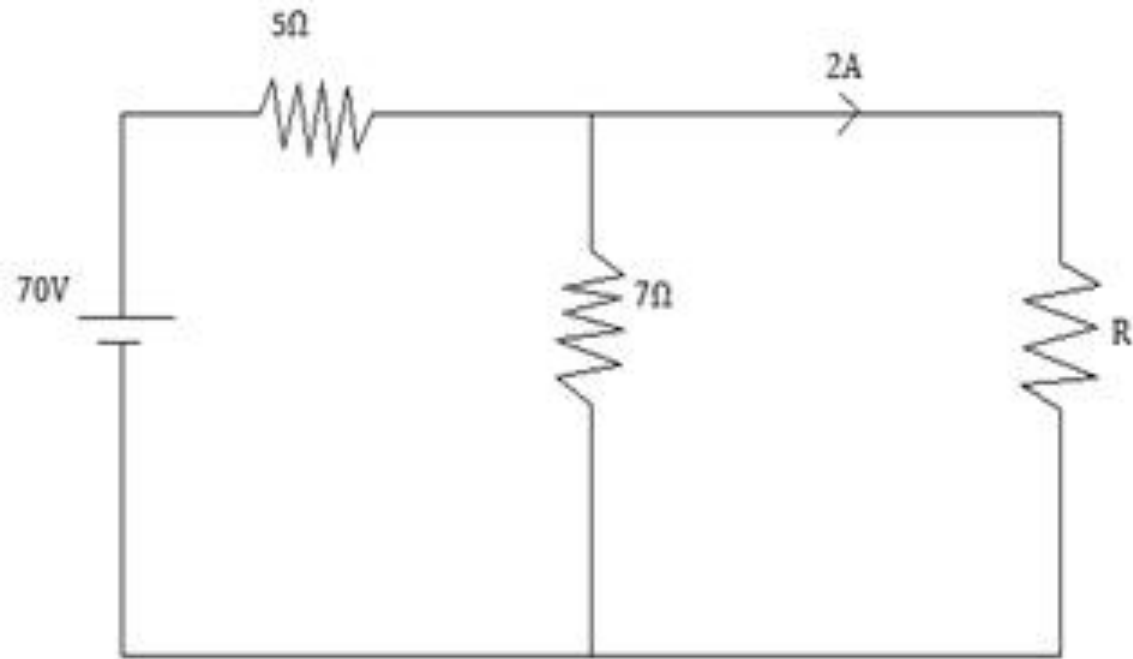- a) $17.5\ \Omega$
- b) $15\ \Omega$
- c) $24\ \Omega$
- d) $10.3\ \Omega$



Answers:

- 1) c
- 2) c
- 3) b&c
- 4) a

Thanks!

Any questions?