







Home My courses Electronics - Fall - 2021/2022 General

For superposition, it is not required that only one independent source be considered at a time; any number of independent

☆ ᢙ

Exam 2- level 2 For all branches on Monday 13/12/2021 from 8:00 pm to 9:30 pm -Note: Don't solve this the exam If your degree 7,8,9 or 10 in exam (1) because you will punish and lost your degree

ᢙ

ß





arked out of

Flag

sources may be considered simultaneously Select one:

- True

uestion 2 ot yet

arked out of

Flag uestion For the circuit in Figure, the voltage divider formula is:



- a. $v_1 = \frac{L_1}{L_1 + L_2} v_s$

Question 3 Not yet

Marked out of 2.00

▼ Flag

A capacitor C "has a charge Q". The actual charges on its plates are:

Select one:

- a. Q,-Q
- O b. Q/2, -Q/2
- O c. Q/2, Q/2
- O d. Q,Q
- O e. Q,0

Question 4

is the property whereby an inductor exhibits opposition to the change of current flowing through it, measured in henrys (H).

Marked out of

Select one:

- ▼ Flag question
- a. Inductance
- O b. resistor
- O c. capacitor
- O d. Capacitance

Question **5** Not yet

Marked out of 2.00

▼ Flag

One of materials listed below is to be placed between two identical metal sheets, with no, air gap, to form a parallel-plate capacitor. Which produces the greatest capacitance?

Select one:

- O a. material of thickness 0.1 mm and dielectric constant 2
- O b. material of thickness 0.2 mm and dielectric constant 3
- c. material of thickness 0.5 mm and dielectric constant 11
- O d material of thickness 0.4 mm and dielectric constant 8
- O e. material of thickness 0.3 mm and dielectric constant 2

Quiz navigation



Finish attempt .

Time left 0:08:48

Finish attempt ...

Learn Any Time, Any Where Hotline: 16541



