



# Physics2


## Section 07

Faculty of Information Technology  
Egyptian E-Learning University

Spring 2021


# Calculation of capacitance

## Isolated charged sphere

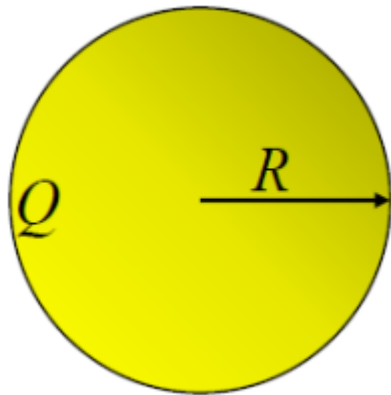

$$C_0 = \frac{R}{k_e} = 4\pi\epsilon_0 R$$

## Parallel Plates

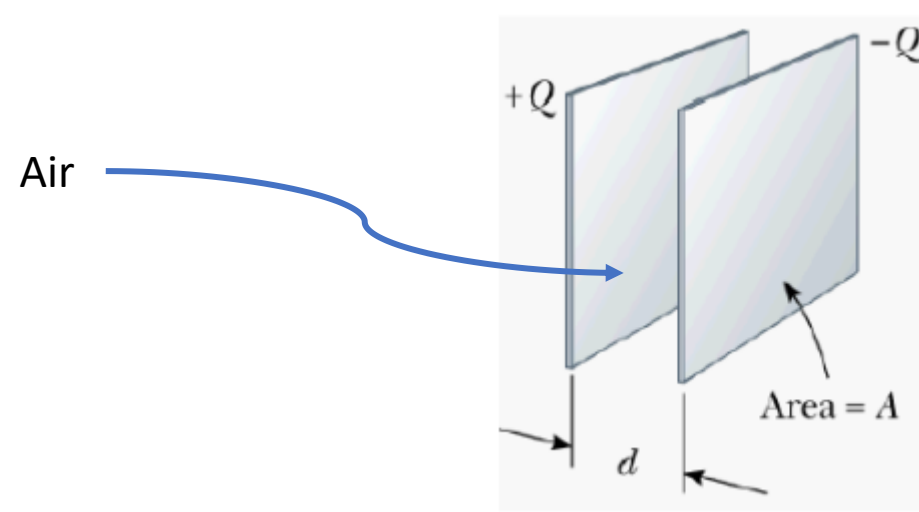

$$C_0 = \frac{\epsilon_0 A}{d}$$

## Q1.

An air-filled spherical capacitor is constructed with inner- and outer-shell radii of **7.00cm** and **14.0cm**, respectively.

- (a) Calculate the capacitance of the device.
- (b) What potential difference between the spheres results in a **4mC** charge on the capacitor?

### Q1.a Solution:

$$C = \frac{|Q|}{|\Delta V|}$$

$$|\Delta V| = |V_1 - V_2| = \left| \frac{k_e Q}{R_1} - \frac{k_e Q}{R_2} \right| = \frac{k_e Q |R_2 - R_1|}{R_2 R_1}$$

$$C = \frac{R_2 R_1}{k_e |R_2 - R_1|} = \frac{0.07 \times 0.14}{8.99 \times 10^9 (0.14 - 0.07)} = 15.58 \text{ PF}$$

### Q1.b Solution:

$$C = \frac{|Q|}{|\Delta V|}$$

$$Q = 4mC, \quad |\Delta V| = \frac{|Q|}{C} = \frac{4 \times 10^{-3}}{15.58 \times 10^{-12}} = 256.86 \text{ MV}$$

## Q2.

An air-filled parallel-plate capacitor has plates of area  **$2.30 \text{ cm}^2$**  separated by  **$1.50 \text{ mm}$** .

- (a) Find the value of its capacitance.
- (b) The capacitor is connected to a 12.0-V battery, What is the charge on the capacitor?
- (c) What is the magnitude of the uniform electric field between the plates?

## Q2 solution.

An air-filled parallel-plate capacitor has plates of area  **$2.30 \text{ cm}^2$**  separated by  **$1.50 \text{ mm}$** .

$$(a) C = \frac{\epsilon_0 A}{d} = \frac{8.85 \times 10^{-12} \times 2.3 \times 10^{-4}}{0.0015} = 1.357 \text{ pF}$$

$$(b) Q = C \times \Delta V = 1.35 \times 10^{-12} \times 12 = 16.28 \times 10^{-12} \text{ C}$$

$$(c) \Delta V = E \cdot d$$

$$E = \frac{\Delta V}{d} = \frac{12}{0.0015} = 8000 \frac{\text{V}}{\text{m}}$$

OR

$$E = \frac{\sigma}{\epsilon_0} = \frac{\frac{Q}{A}}{\epsilon_0} = 70.783 \times \frac{10^{-9}}{8.85 \times 10^{-12}} = 7998.03 \approx 8000 \text{ V/m}$$

# Combinations of capacitors

In parallel, the **potential difference is the same** across all capacitors.

$$C_{eq} = C_1 + C_2 + C_3 + \dots$$


in series, the **charge is the same** on all capacitors.

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

## Q1

For the system of four capacitors shown in the Figure, find

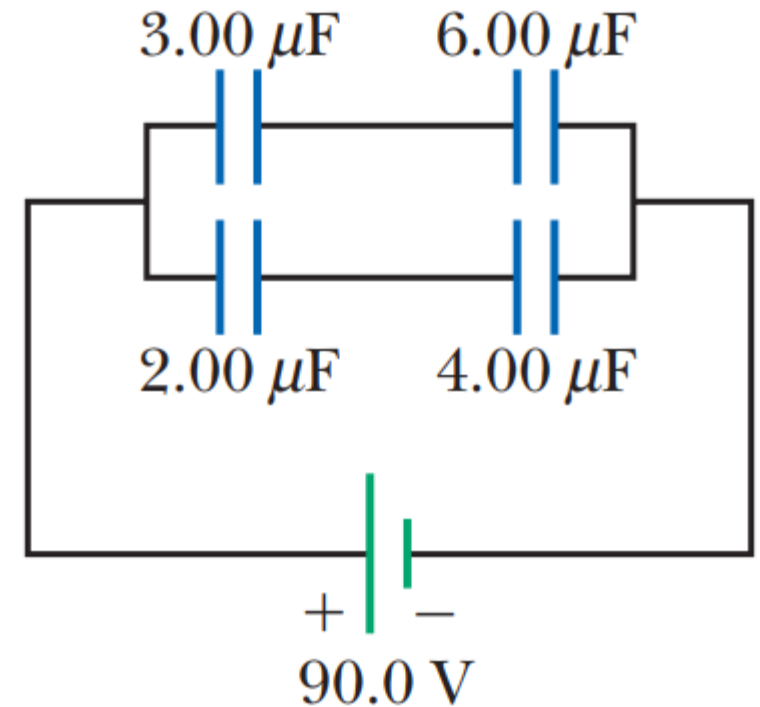- a) the equivalent capacitance of the system.
- b) The charge on each capacitor.
- c) the potential difference across each capacitor





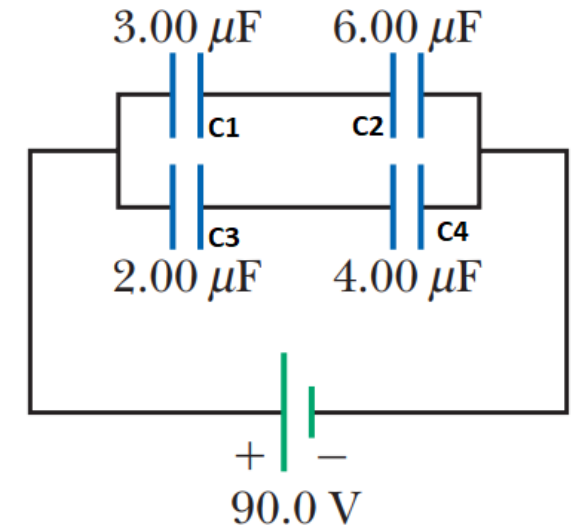
## Q1.solution

a)

$$C_a = \frac{C_1 C_2}{C_1 + C_2} = 2 \mu F$$
$$C_b = \frac{C_3 C_4}{C_3 + C_4} = \frac{4}{3} = 1.33 \mu F$$
$$C_{eq} = C_a + C_b = 3.33 \mu F$$




b)

$$Q_a = Q_1 = Q_2 = \Delta V \times C_a = 90 \times 2 \times 10^{-6} = 180 \mu C$$
$$Q_b = Q_3 = Q_4 = \Delta V \times C_b = 90 \times \frac{4}{3} \times 10^{-6} = 120 \mu C$$

c)
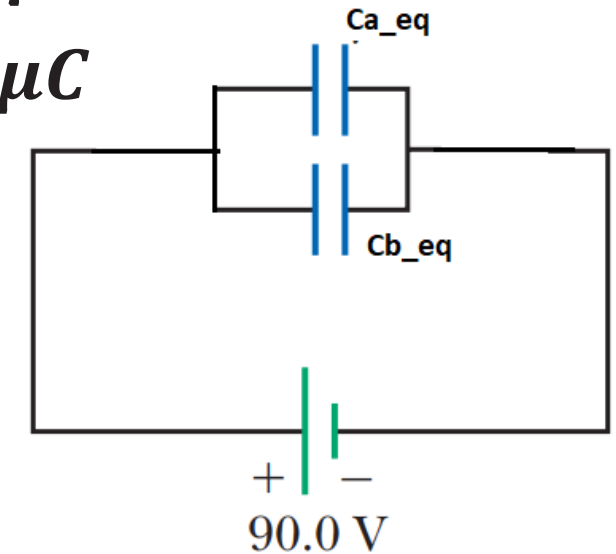
$$\Delta V_1 = \frac{Q_1}{C_1} = \frac{180 \mu C}{3 \mu F} = 60 V, \Delta V_2 = \frac{180}{6} = 30 V$$
$$\Delta V_3 = \frac{120}{2} = 60 V, \Delta V_4 = \frac{120}{4} = 30 V$$



## Capacitors with any dielectric

$$C = kC_0$$

K is a dimensionless factor , called the **dielectric constant** where  $C_0$  is the capacitance in the absence of the dielectric

## Q1

How much charge can be placed on a capacitor with air between the plates before it breaks down (Air:  $E_{max} = 3 \times 10^6 \text{ V/m}$ ) if the area of each plate is **5.00 cm<sup>2</sup>**?

**What If?** Find the maximum charge if **polystyrene** ( $E_{max} = 24 \times 10^6 \text{ V/m}$ ,  $k=2.56$ ) is used between the plates instead of air.

## Q1.solution

$$a) C_{air} = \frac{Q}{\Delta V} = \frac{\epsilon_0 A}{d} = \frac{Q}{E \times d},$$

$$\text{so } Q_{air(max)} = \epsilon_0 A E_{max} = 8.85 \times 10^{-12} \times 5 \times 10^{-4} \times 3 \times 10^6 \\ = 13.3 \text{ nC}$$

$$b) C_{poly} = \frac{k_{poly} \cdot \epsilon_0 \cdot A}{d} = \frac{Q_{max}}{E_{max} \cdot d}$$

$$Q_{poly(max)} = k_{poly} \cdot \epsilon_0 \cdot A \cdot E_{max} = 2.56 \times 8.85 \times 10^{-12} \times 5 \times 10^{-4} \\ \times 24 \times 10^6 = 271.9 \text{ nC}$$

## Energy stored in charged capacitor

$$U_E = \frac{Q^2}{2C} = \frac{1}{2}Q\Delta V = \frac{1}{2}C(\Delta V)^2$$

## Q1

Two capacitors,  $C1 = 18.0 \mu F$  and  $C2 = 36.0 \mu F$ , are connected in series, and a 12.0-V battery is connected across the two capacitors. Find

- (a) the equivalent capacitance
- (b) the energy stored in this equivalent capacitance.
- (c) Find the energy stored in each individual capacitor.
- (d) Show that the sum of these two energies is the same as the energy found in part (b).
- (e) If the same capacitors were connected in parallel, what potential difference would be required across them so that the combination stores the same energy as in part (a)?
- (f) Which capacitor stores more energy in this situation,  $C1$  or  $C2$ ?

## Q1 .Solution

$$(a) C_{eq( Series)} = \frac{C_1 C_2}{C_1 + C_2} = \frac{18 \times 36}{18 + 36} = 12 \mu F$$

$$(b) U = 0.5 \times C_{eq} \times V^2 = 864 \mu J$$

$$(c) U_1 = 0.5 \times \frac{Q_1^2}{C_1}$$

$$Q_1 = Q_{eq} = C_{eq} \times \Delta V = 12 \times 10^{-6} \times 12 = 144 \mu C$$

$$U_1 = \frac{(144 \times 10^{-6})^2}{2 \times 18 \times 10^{-6}} = 675 \mu J, \quad U_2 = \frac{(144 \times 10^{-6})^2}{2 \times 36 \times 10^{-6}} = 288 \mu J.$$

$$d) U_1 + U_2 = 864 \mu J = U_{total} (from b).$$

$$e) U = 0.5 \times C_{eq} \times V^2 = 864 \mu J$$

$$C_{eq} = C_1 + C_2 = 54 \mu F, V( required ) = \sqrt{\frac{2 \times 864}{54}} = 5.66 V$$

$$f) \text{ In parallel connection } \Delta V_1 = \Delta V_2,$$

*since  $U = 0.5 \times C \times \Delta V^2$ ,  $U_2$  will be greater than  $U_1$  as  $C_2 > C_1$*

## MCQ

1) By what factor is the capacitance of a metal sphere multiplied if its volume is tripled?

(a) 3

(b)  $3^{1/3}$

(c) 1

(d)  $3^{-\frac{1}{3}}$

(e)  $\frac{1}{3}$

Ans.(b)