


Electronics Section 05

Faculty of Information Technology Egyptian
E-Learning University
Sadat Center & Assiut Center
Fall 2021


by Mohamed khalifa & Ahmed Abdel-Rahim

Thevenin's Theorem

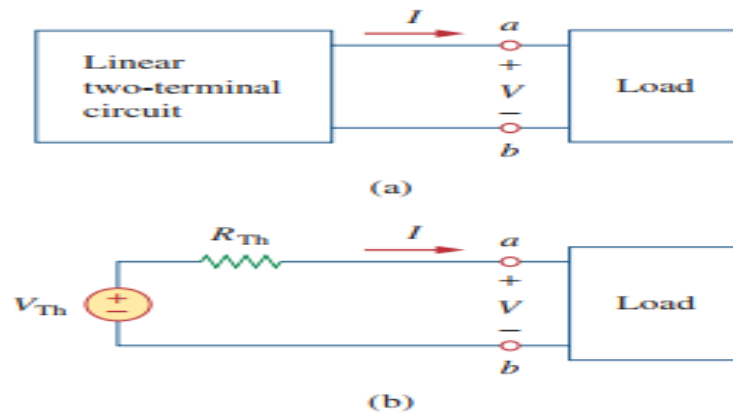Thevenin's theorem states that a linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{Th} in series with a resistor R_{Th} , where V_{Th} is the open-circuit voltage at the terminals and R_{Th} is the input or equivalent resistance at the terminals when the independent sources are turned off.



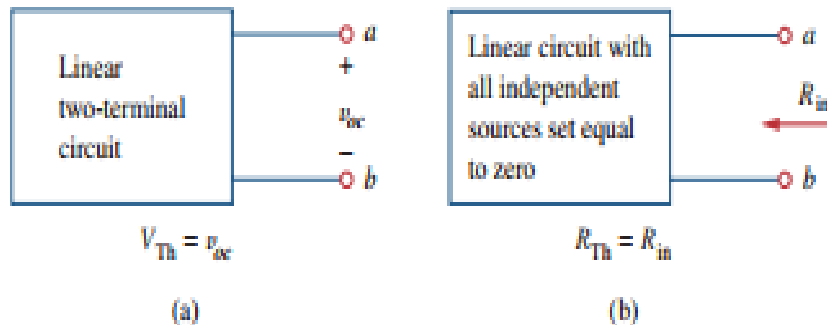Replacing a linear two-terminal circuit by its Thevenin equivalent: (a) original circuit, (b) the Thevenin equivalent circuit.



$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

$$V_L = R_L I_L = \frac{R_L}{R_{Th} + R_L} V_{Th}$$

Maximum Power Transfer

Maximum power is transferred to the load when the load resistance equals the Thevenin resistance as seen from the load ($R_L = R_{Th}$).

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

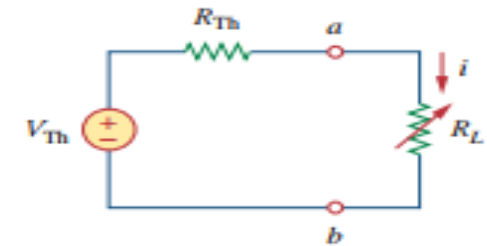


Figure
The circuit used for maximum power transfer.


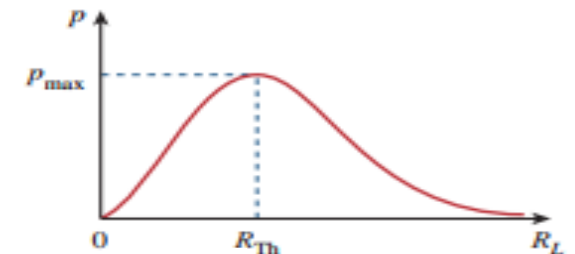




Figure
Power delivered to the load as a function of R_L .

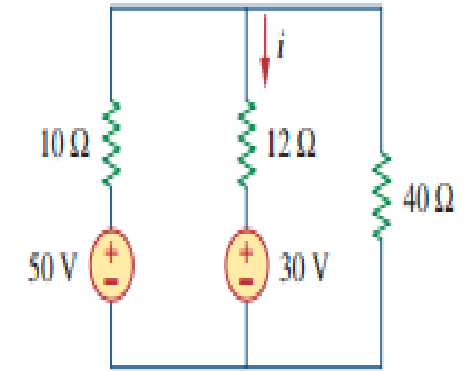Q1. Solve for the current i in the circuit of Figure using Thevenin's theorem. (*Hint:* Find the Thevenin equivalent seen by the $12\text{-}\Omega$ resistor.)




Solution

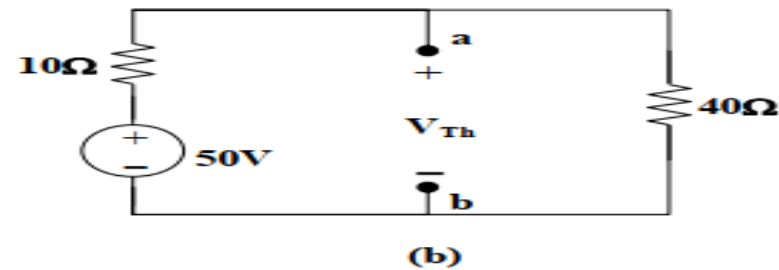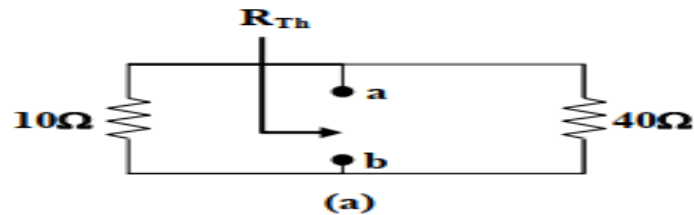Remove the 30-V voltage source and the 20-ohm resistor.



From Fig. (a), $R_{Th} = 10 \parallel 40 = 8 \text{ ohms}$

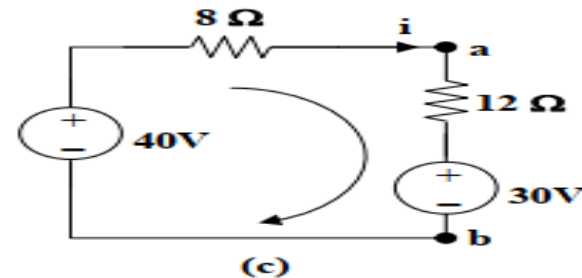
From Fig. (b), $V_{Th} = (40/(10 + 40))50 = 40\text{V}$



The equivalent circuit of the original circuit is shown in Fig. (c). Applying KVL,


$$30 - 40 + (8 + 12)i = 0, \text{ which leads to } i = 500\text{mA}$$

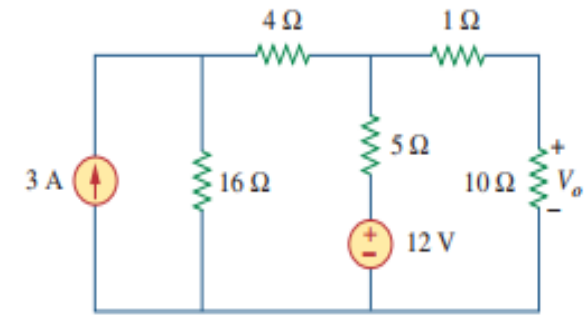Q2. Apply Thevenin's theorem to find V_o in the circuit of Figure.




Solution

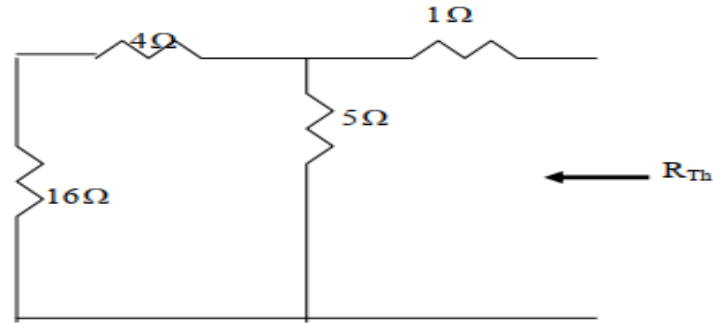We find Thevenin equivalent at the terminals of the 10-ohm resistor. For R_{Th} , consider the circuit below.



$$R_{Th} = 1 + 5 // (4 + 16) = 1 + 4 = 5\Omega$$

For V_{Th} , consider the circuit below.

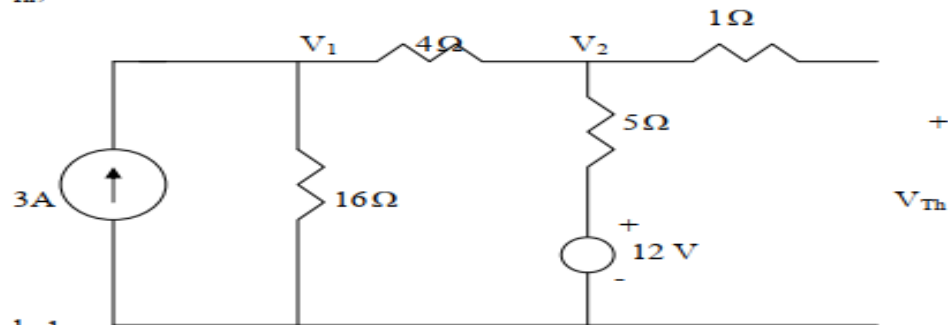

At node 1,

$$3 = \frac{V_1}{16} + \frac{V_1 - V_2}{4} \longrightarrow 48 = 5V_1 - 4V_2 \quad (1)$$


At node 2,

$$\frac{V_1 - V_2}{4} + \frac{12 - V_2}{5} = 0 \longrightarrow 48 = -5V_1 + 9V_2 \quad (2)$$

Solving (1) and (2) leads to

$$V_{Th} = V_2 = 19.2$$

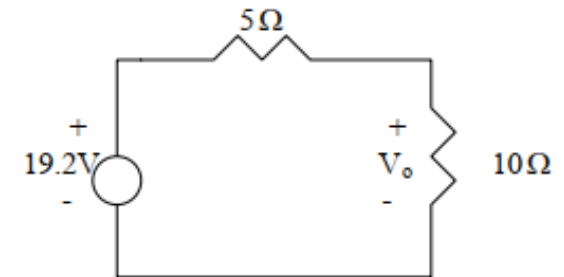
Thus, the given circuit can be replaced as shown below.



Using voltage division,


$$V_o = \frac{10}{10 + 5} (19.2) = 12.8 \text{ V.}$$

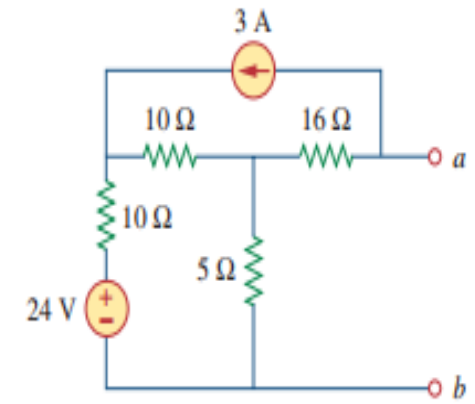Q3. Obtain the Thevenin equivalent at terminals of the circuit shown in Figure




Solution

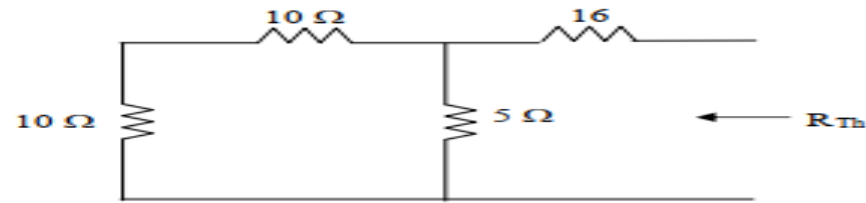We obtain R_{Th} using the circuit below.



$$R_{Th} = 16 + (10 \parallel 5) = 16 + (10 \times 5) / (10 + 5) = 20 \Omega$$

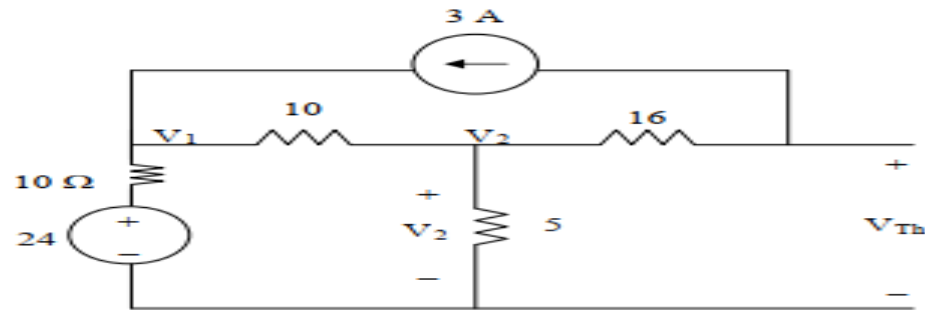To find V_{Th} , we use the circuit below.



At node 1,

$$\frac{24 - V_1}{10} + 3 = \frac{V_1 - V_2}{10} \longrightarrow 54 = 2V_1 - V_2 \quad (1)$$

At node 2,

$$\frac{V_1 - V_2}{10} = 3 + \frac{V_2}{5} \longrightarrow 60 = 2V_1 - 6V_2 \quad (2)$$


Subtracting (1) from (2) gives

$$6 = -5V_2 \text{ or } V_2 = -1.2 \text{ V}$$

But



$$-V_2 + 16 \times 3 + V_{Th} = 0 \text{ or } V_{Th} = -(48 + 1.2) = -49.2 \text{ V}$$

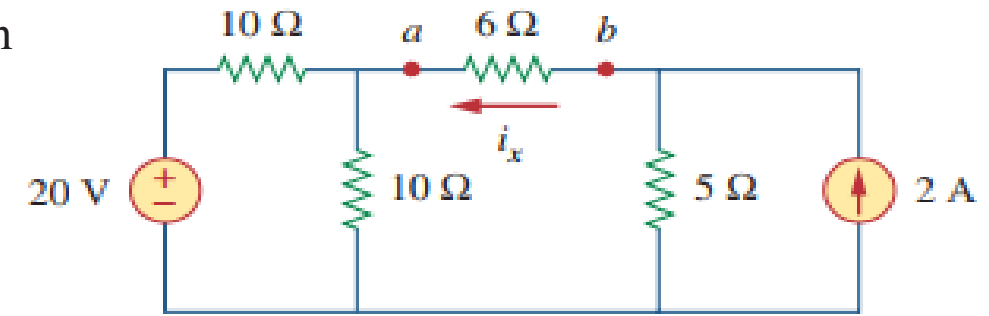Q4. Find the Thevenin equivalent looking into terminals a - b of the circuit in Figure and solve for i_x .



Solution

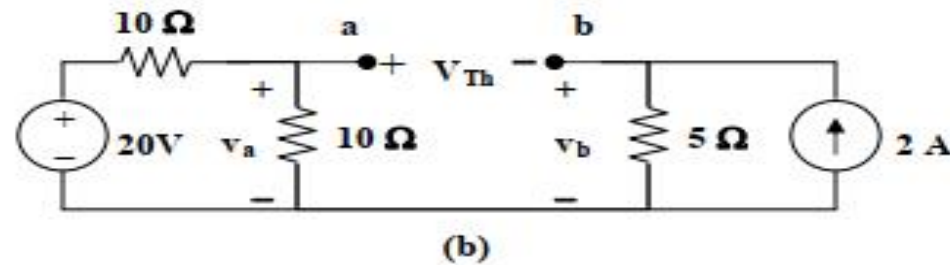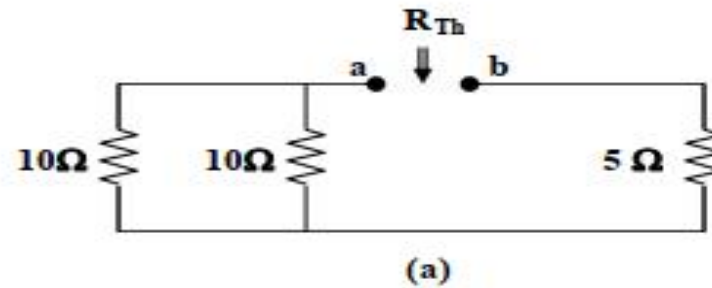To find R_{Th} , consider the circuit in Fig. (a).




$$R_{Th} = 10 \parallel 10 + 5 = 10 \text{ ohms}$$

To find V_{Th} , consider the circuit in Fig. (b).

$$v_b = 2 \times 5 = 10 \text{ V}, \quad v_a = 20/2 = 10 \text{ V}$$


$$\text{But, } -v_a + V_{Th} + v_b = 0, \text{ or } V_{Th} = v_a - v_b = 0 \text{ volts}$$

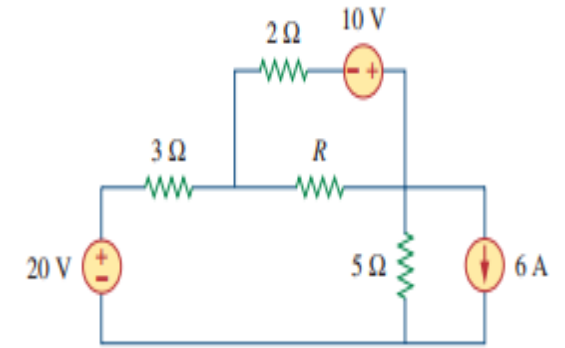Q5. Find the maximum power that can be delivered to the resistor R in the circuit of Figure.



Solution

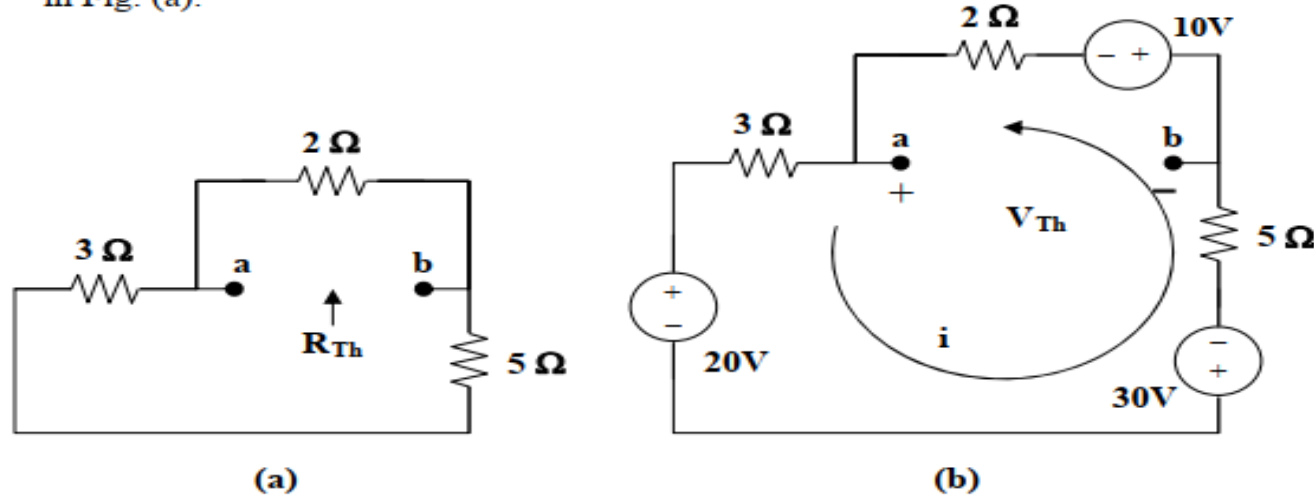We first find the Thevenin equivalent at terminals a and b. We find R_{Th} using the circuit in Fig. (a).



$$R_{Th} = 2 \parallel (3 + 5) = 2 \parallel 8 = \mathbf{1.6 \text{ ohms}}$$

By performing source transformation on the given circuit, we obtain the circuit in (b). We now use this to find V_{Th} .


$$10i + 30 + 20 + 10 = 0, \text{ or } i = -6$$

$$V_{Th} + 10 + 2i = 0, \text{ or } V_{Th} = 2 \text{ V}$$

$$p = V_{Th}^2 / (4R_{Th}) = (2)^2 / [4(1.6)] = \mathbf{625 \text{ m watts}}$$

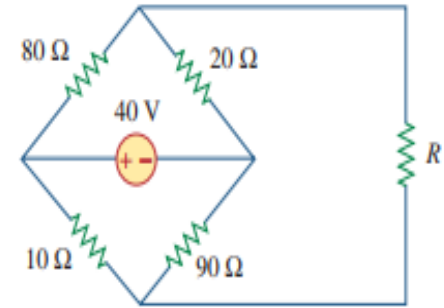
Q6. The variable resistor R in Figure is adjusted until it absorbs the maximum power from the circuit.

- Calculate the value of R for maximum power.
- Determine the maximum power absorbed by R .




Solution

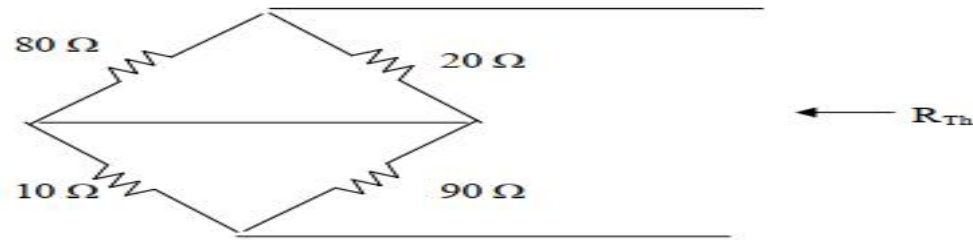We first find the Thevenin equivalent. We find R_{Th} using the circuit below.



$$R_{Th} = 20 // 80 + 90 // 10 = 16 + 9 = 25 \Omega$$

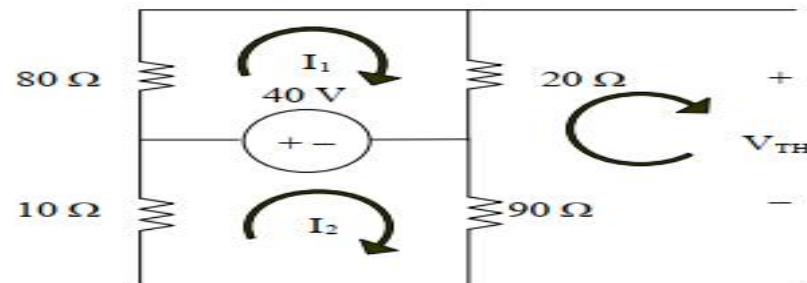We find V_{Th} using the circuit below. We apply mesh analysis.




$$\begin{aligned} (80 + 20)i_1 - 40 &= 0 & \longrightarrow & i_1 = 0.4 \\ (10 + 90)i_2 + 40 &= 0 & \longrightarrow & i_2 = -0.4 \\ -90i_2 - 20i_1 + V_{Th} &= 0 & \longrightarrow & V_{Th} = -28 \text{ V} \end{aligned}$$

(a) $R = R_{Th} = 25 \Omega$

(b) $P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(28)^2}{100} = 7.84 \text{ W}$

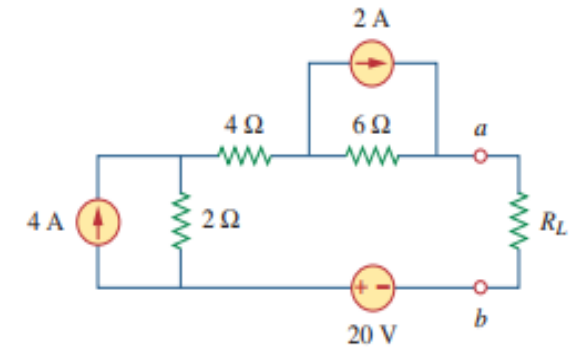- Q7.** (a) For the circuit in Figure, obtain the Thevenin equivalent at terminals a-b
 (b) Calculate the current in $R_L = 8 \Omega$.
 (c) Find for maximum power deliverable to R_L .
 (d) Determine that maximum power.





Solution

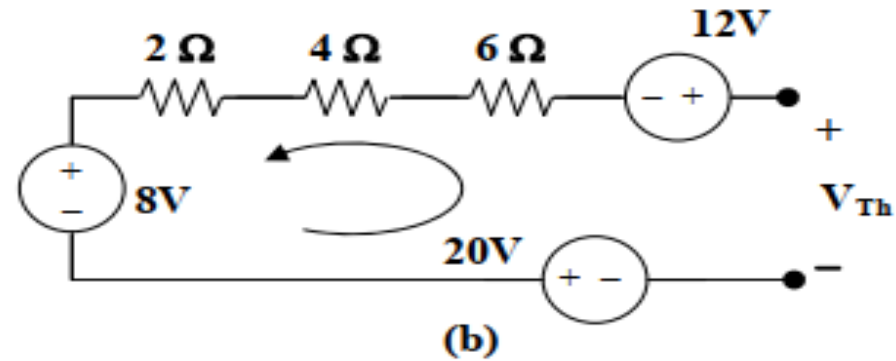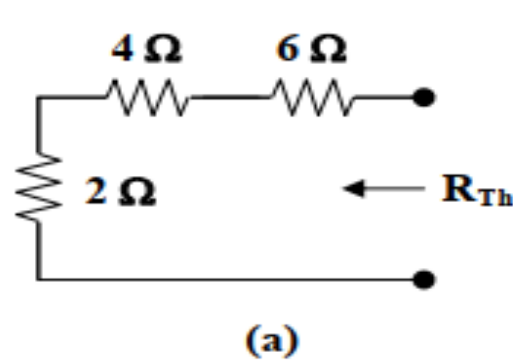(a) R_{Th} and V_{Th} are calculated using the circuits shown in Fig. (a) and (b) respectively.

From Fig. (a), $R_{Th} = 2 + 4 + 6 = 12 \text{ ohms}$

From Fig. (b), $-V_{Th} + 12 + 8 + 20 = 0$, or $V_{Th} = 40 \text{ V}$




(b) $i = V_{Th} / (R_{Th} + R) = 40 / (12 + 8) = 2 \text{ A}$

(c) For maximum power transfer, $R_L = R_{Th} = 12 \text{ ohms}$


(d) $p = V_{Th}^2 / (4R_{Th}) = (40)^2 / (4 \times 12) = 33.33 \text{ watts.}$

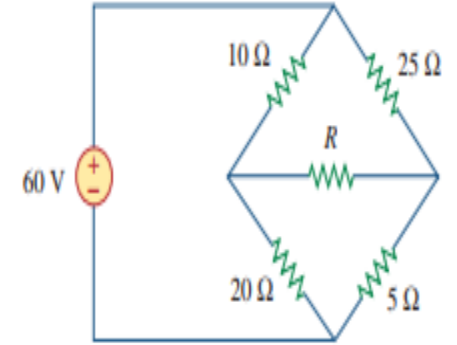Q8. Determine the maximum power that can be delivered to the variable resistor R in the circuit of Figure.




Solution

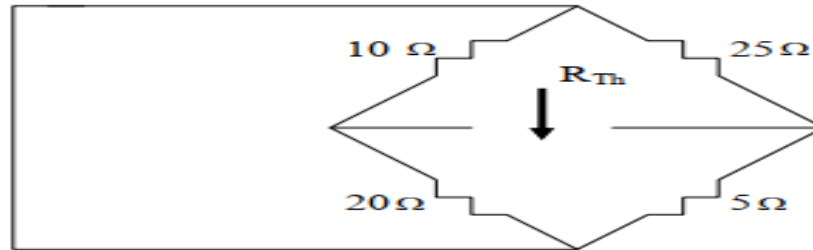Find the Thevenin's equivalent circuit across the terminals of R .


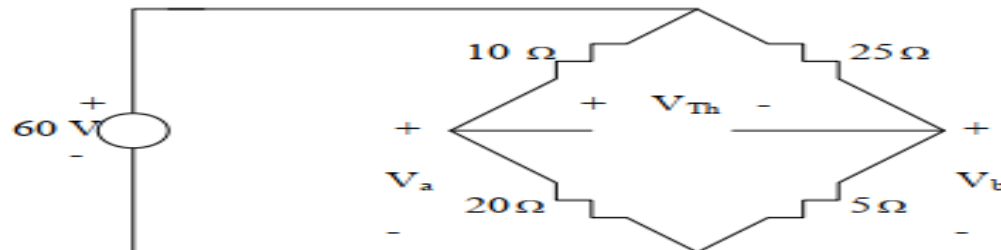
$$R_{Th} = 10 // 20 + 25 // 5 = 325 / 30 = 10.833 \Omega$$



$$V_a = \frac{20}{30}(60) = 40, \quad V_b = \frac{5}{30}(60) = 10$$

$$-V_a + V_{Th} + V_b = 0 \quad \longrightarrow \quad V_{Th} = V_a - V_b = 40 - 10 = 30 \text{ V}$$

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{30^2}{4 \times 10.833} = 20.77 \text{ W.}$$